# CA Assignment - 2 Serial Bus

Serial bus system - It has 6 registers each can store 4 bits of data.

Other components used are - 3x8 decoders, 2x1 Mux, OR gates, etc.

To transfer data from one register to another(bit-wise), we have implemented a serial bus.

Variables: - A, B, C, D, A', B', C'.

#### Step - 1:- To load registers

- ➤ Initially all the variables(A,B,C,D,A',B',C') must be set to 0.
- ➤ Then, provide inputs to the registers(Input 0 to Input 5).
- ➤ Change the clock cycle.

  Finally values will be loaded to all the registers.

## Step - 2:- To transfer values.


- > Now set D as 1.
- ➤ Select the source register using the variables A, B, C. (Change value at 2 place)
- > Select the destination register using the variables A', B', C'.
- ➤ Change the clock cycle.

  Finally the source value will reach the destination.


In this system single bit is transfered,

Thus, at the source circular shift will take place and at destination shift operation will occur(on the basis of the source bit transferred)
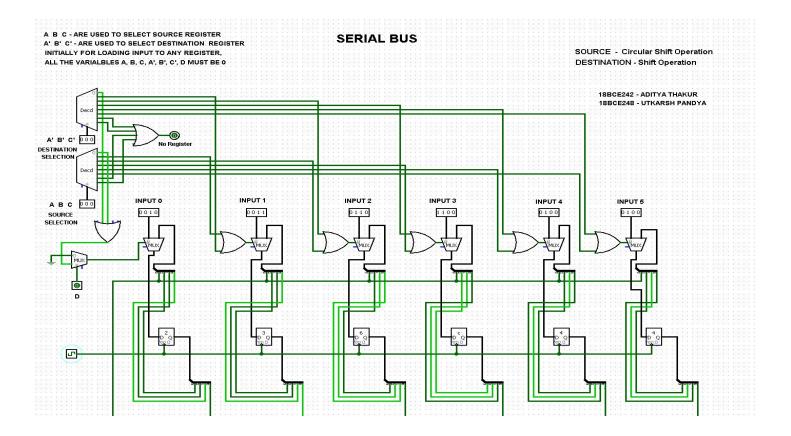
### ➤ <u>Values are loaded into the registers.</u>



# > After the Shift Operation

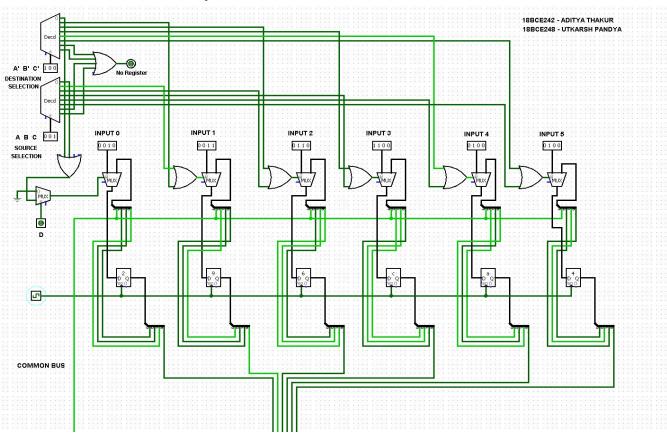

#### Example (From above image) :-

```
Initial value in Register 0 :- 2 (0010)
Initial value in Register 1 :- 3 (0011)
Initial value in Register 2:- 6 (0110)
Initial value in Register 3 :- C (1100)
Initial value in Register 4 :- 4 (0100)
Initial value in Register 5 :- 4 (0100)
Variable:-
   ➤ Source : ABC - 001 (Reg - 1)
   > Destination : A'B'C' - 100 (Reg - 4)
   ➤ Means transferring the least significant bit of Reg-1 to Reg-4
Register 0 :- 2 (0010) No change
Register 1:- 9 (1001) Circular shift operation in source(Reg - 1)
Register 2:- 6 (0110) No change
Register 3:- C (1100) No change
Register 4:- A (1010) source bit(Reg - 1) is transferred to destination(Reg - 4)
Register 5 :- 4 (0100) No change
```